

## L: Solve Combined Circuits in One-Step

### Level 6

Prerequisite: Solve Complete Circuits with Nontraditional Information

Points To:

### Objectives

- Solve for the voltage, current, resistance, and power of each element of a circuit that combines series and parallel elements.
- Use the “accordion method” of creating simpler circuits and using them to understand more complicated circuits.
- Use the formulas for combining resistance in series and parallel. (Especially practice the fractions in the parallel circuit formula!)

### Limits:

- All of the circuits have only one step of simplification. They are only series in parallel or parallel in series, never any more complicated circuit.
- Every circuit has only one battery.
- Information provided is always the voltage of the battery

Step 1:

Combine the resistors using the correct formula until you have a simple circuit.

Equivalent Resistance for a Series Circuit	Equivalent Resistance for a Parallel Circuit
$R_s = R_1 + R_2 + R_3$	$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$

Step 2:

Solve the simple circuit.

Step 3:

Go upward to each complex circuit, one at a time. In each case, follow the rule for separating resistors.

Rule for separating two resistors in series	Rule for separating two resistors in parallel.
Two resistors in series <i>always have the same current.</i>	Two resistors in parallel <i>always have the same voltage (potential difference).</i>

Step 4:

Solve each more complex circuit as you reach it.

Repeat.

Step 5:

Use the information you have compiled to answer the final question:


Problem 1:  
 Using the table below, find the power dissipated by each individual resistor and the total circuit:

Original Circuit					
		V			
		I			
		R			
		P			
Simpler Circuit		V			
		I			
		R			
		P			

Final Answer:

	Resistor A	Resistor B	Resistor C	Total Circuit
Power (Watts)				


**Problem 2:** Using the table below, find the power dissipated by each individual resistor and the total circuit:

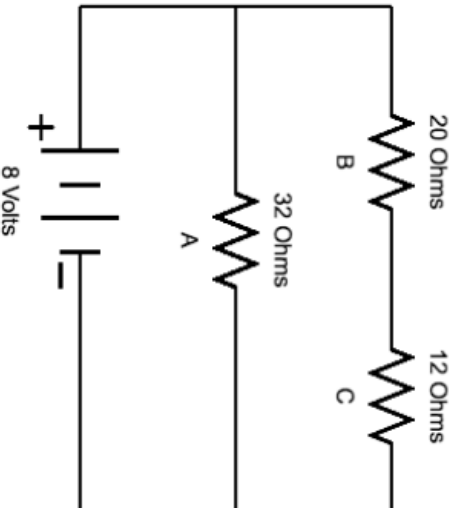Original Circuit						
						
V						
I						
R						
P						
Simpler Circuit						
V						
I						
R						
P						

Final Answer:

	Resistor A	Resistor B	Resistor C	Total Circuit
Power (Watts)				


**Problem 3:** Using the table below, find the power dissipated by each individual resistor and the total circuit:

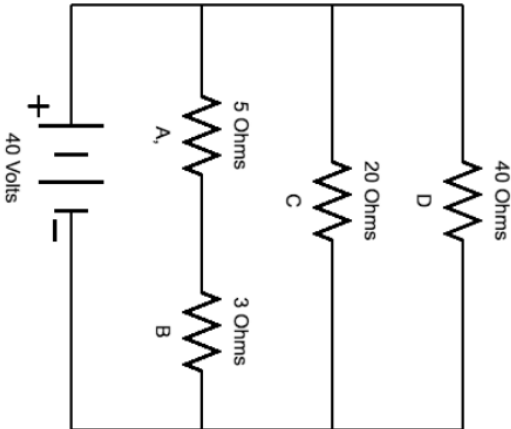Original Circuit							
							
V							
I							
R							
P							
Simpler Circuit		V					
		I					
		R					
		P					

Answer the final question

	Resistor A	Resistor B	Resistor C	Resistor D	Total Circuit
Power (Watts)					


**Problem 4:** Using the table below, find the power dissipated by each individual resistor and the total circuit:
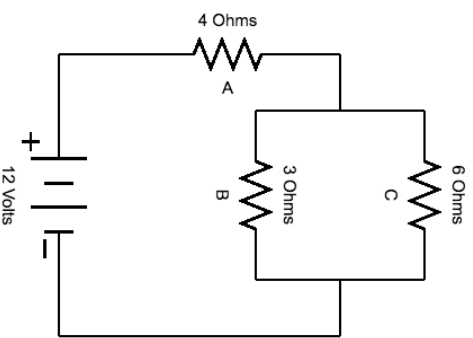
<div>Original Circuit</div> 					
	V				
	I				
	R				
	P				
<div>Simpler Circuit</div>	V				
	I				
	R				
	P				

	Resistor A	Resistor B	Resistor C	Total Circuit
Power (Watts)				

**Problem 4:**

Using the table below, find the power dissipated by each individual resistor and the total circuit:

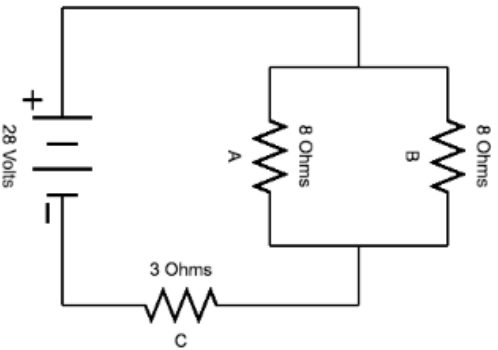Original Circuit 					
	V				
	I				
	R				
	P				
Simpler Circuit	V				
	I				
	R				
	P				

	Resistor A	Resistor B	Resistor C	Total Circuit
Power (Watts)				

## Answers

1.

	Resistor A	Resistor B	Resistor C	Total Circuit
Power (Watts)	64	128	96	288

2.

	Resistor A	Resistor B	Resistor C	Total Circuit
Power (Watts)	2	1.25	0.75	4

3.

	Resistor A	Resistor B	Resistor C	Resistor D	Total Circuit
Power (Watts)	125	75	80	40	320

4.

	Resistor A	Resistor B	Resistor C	Total Circuit
Power (Watts)	48	32	32	112



One-Step Accordion Problem Template

Original Circuit		V				
		I				
		R				
		P				
Simpler Circuit		V				
		I				
		R				
		P				

Alternative one-step accordion method template

Original Circuit					
	V				
	I				
	R				
	P				
Simpler Circuit	V				
	I				
	R				
	P				